

# Analog Bass Drum workshop

© Caspar Ockeloen-Korppi



23.11.2015

Helsinki Sound-electronics

In this workshop we will build a classic analog drum circuit. First we will build up the circuit step-by-step on the breadboard, then have a short look at how it works.


## Materials needed

- Breadboard, wires, 9V battery and battery clip
- 1 x LM358 (dual operational amplifier)
- Capacitors: 1 x 10  $\mu$ F, 4 x 100 nF
- Resistors: 2 x 220 Ohm, 1 x 4.7k, 5 x 10k, 1 x 47k, 2 x 470k, 1 x 1M
- Diode: 1 x 1N4148
- Potentiometers: 1 x 10k, 1 x 100k (or 1M)

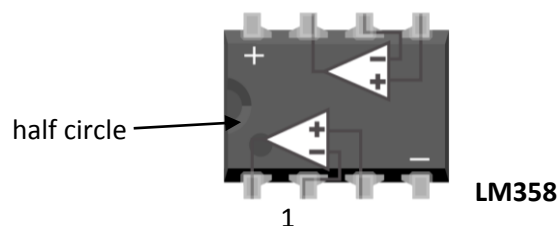
## Opamp chip

The circuit needs only one IC, an “operational amplifier” or simply opamp. They come in many varieties, and we will use the LM358, which contains 2 opamps in a single chip.


Here is the pinout of the LM358. Notice the orientation of the chip: on the left side there is a half circle indentation.



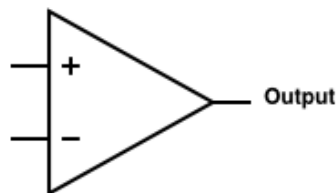I have drawn the opamp circuit symbols on top of the chip for clarity. Each amplifier is drawn as a triangle, with two inputs (+ and -) and one output. The schematic symbol of an opamp is:



**Note:** You can also use some other opamp chips. LM324 is a good alternative, it is just like LM358, but has 4 amplifiers instead of 2. On the right is the pinout of LM324 – be careful that the power pins (+ and -) are different! If you use LM324, you will have to change the bread board layout.

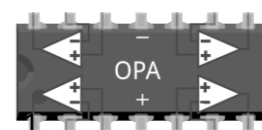

LM324

## Step 1: Power voltages

First set up the power 'rails' of the breadboard. The battery gives us only 2 voltages (9V and 0V), but we need 3. We will use 2 resistors and one opamp to make the third voltage,  $V_{ref} = 4.5\text{ V}$ .


- Connect the clip (**not yet the battery!**) to the top power rail (red = 9V, blue = 0V), and connect only the 0V rail through to the bottom blue one (blue = 0V).

**Note:** some breadboards have 'split' supply rails. If yours does, connect the left and right half together with 4 small wires (see picture).

- Place the opamp in the middle, and connect power (pin 8) and ground (pin 4) as shown.


**Note:** the half circle indent on the chip is on the left.

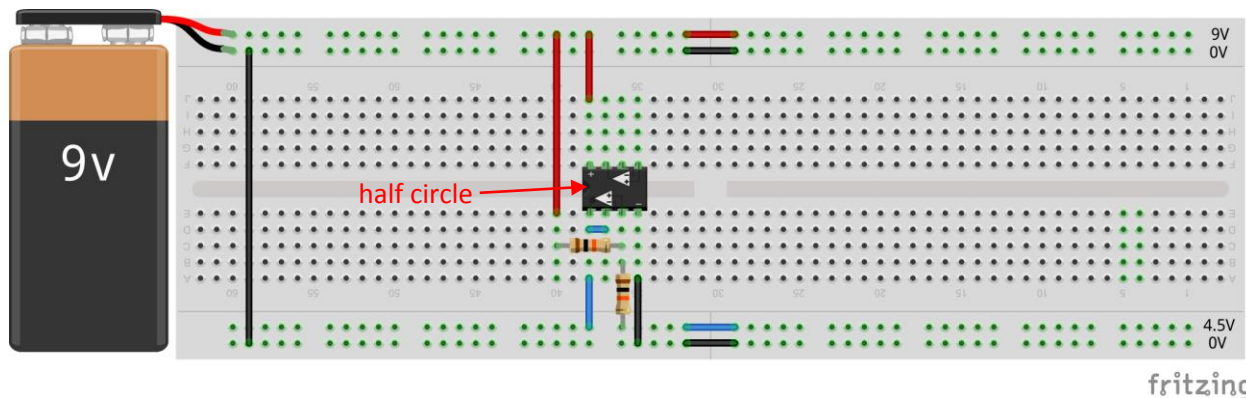
- Wire up the opamp as shown, with two 10 kOhm resistors (from 9V to +, from + to 0V) and some wires.




Now you have 3 power rails. Connect the battery, and use the multimeter to check you have 9V and 4.5V with respect to ground (0V). **Now disconnect the battery again for the next step.**

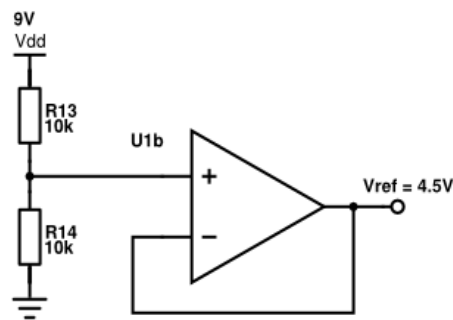Here is the schematic for creating  $V_{ref}$ :



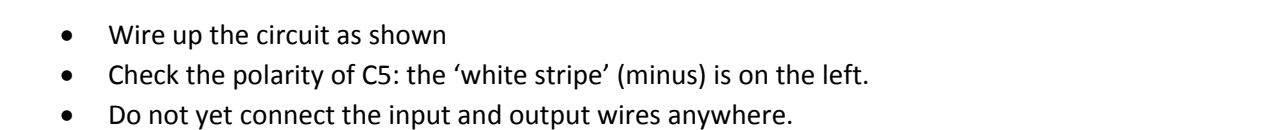


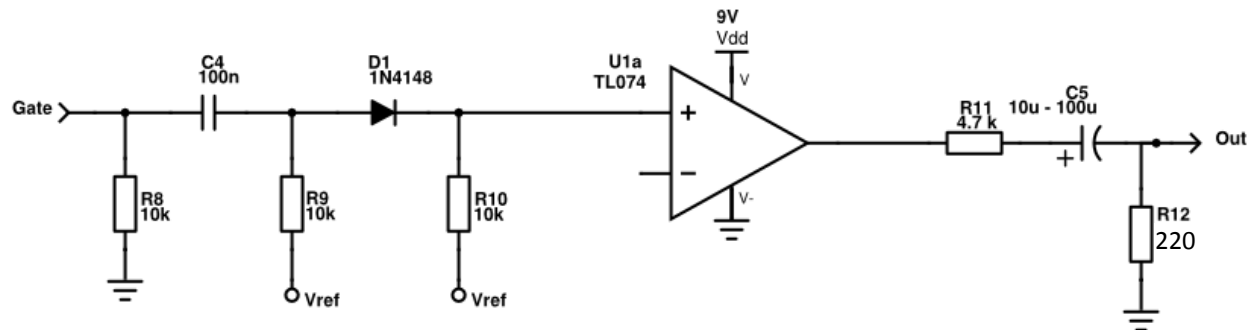- Below is the schematic. The left section is the input, the right part is the output.



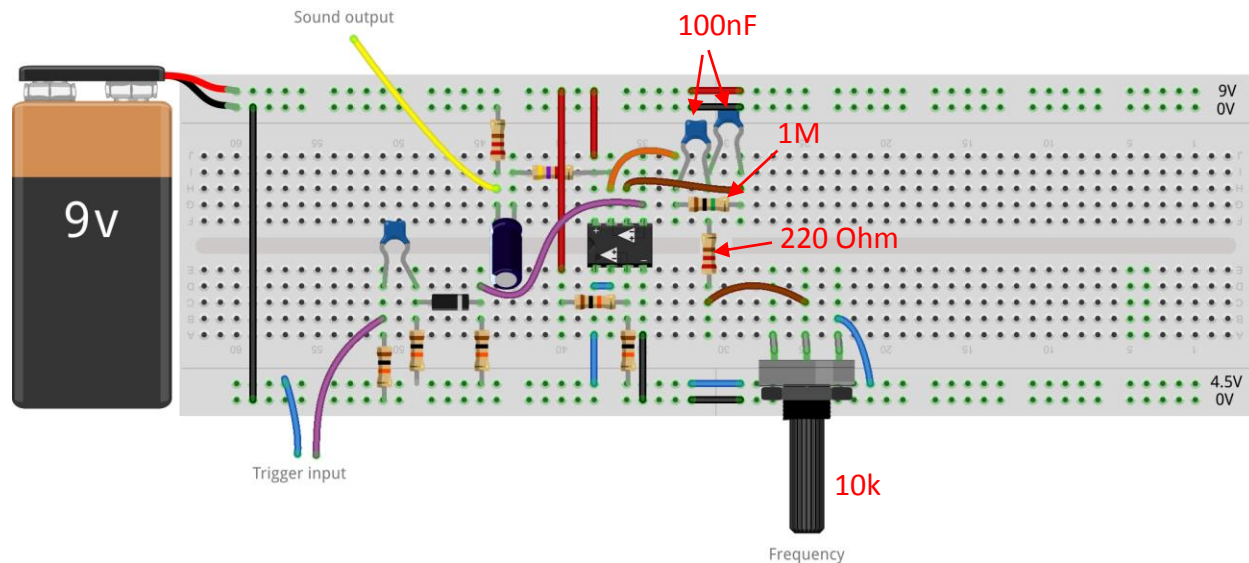
## Step 3: Basic drum

Now it's time to make some drums! This is the heart of the circuit: a filter between the output and – input of the opamp.



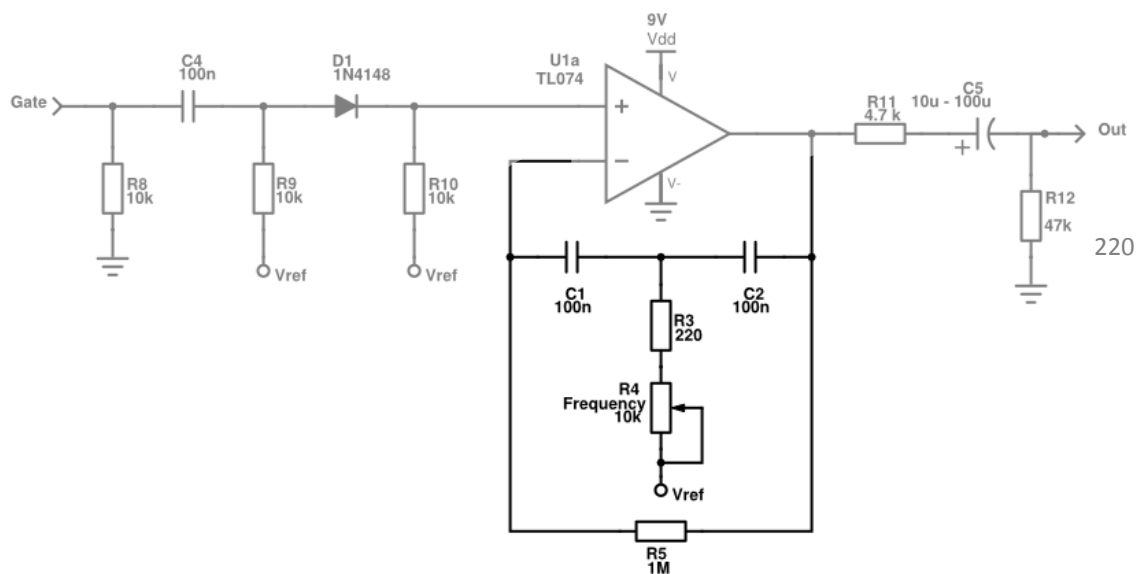Here is the schematic. Note that one leg of the potentiometer goes to 4.5V (Vref):




Now connect the output to an amplifier and loudspeaker, and plug in the battery. To kick the drum, touch the input wires (purple & blue) together. You should hear a short drum sound, and the frequency knob changes it from very low frequency (inaudible) to kind of a 'tom' sound.

**If you are connecting this at home, read the connection tips at the end of the document first!**


**Tip:** If you hear a continuous tone or noise, try adding an extra 100nF capacitor between the opamp '+' and '-' power pins (pin 4 and pin 8). Also make the wires added in this step as short as possible.
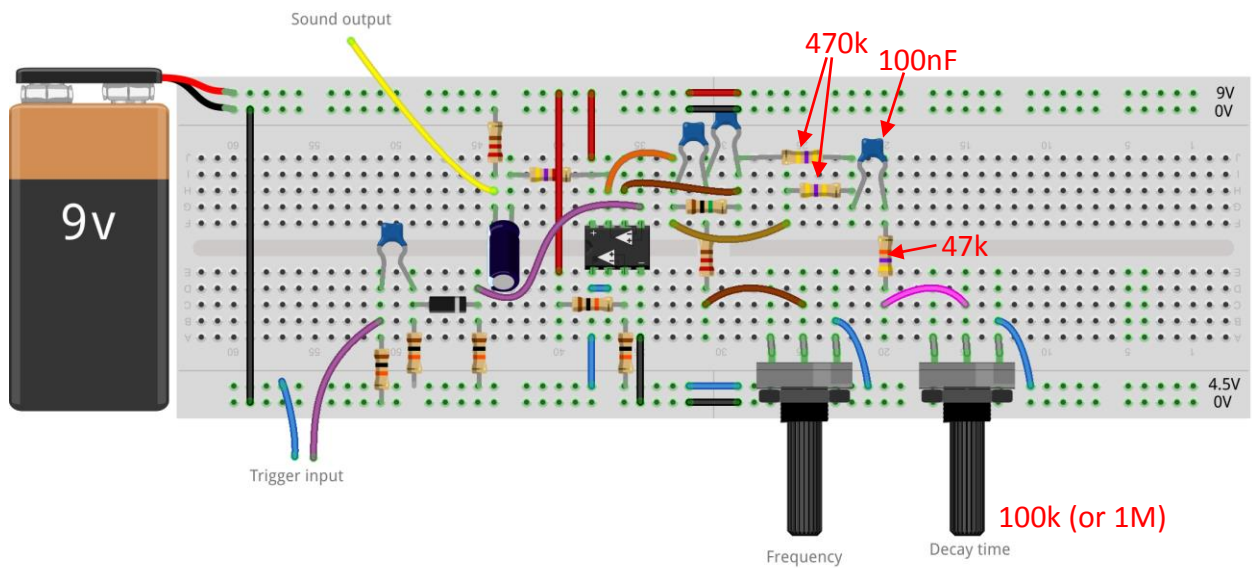
## Step 4: Decay time

The final addition is to make a variable decay time with a second potentiometer:




fritzing

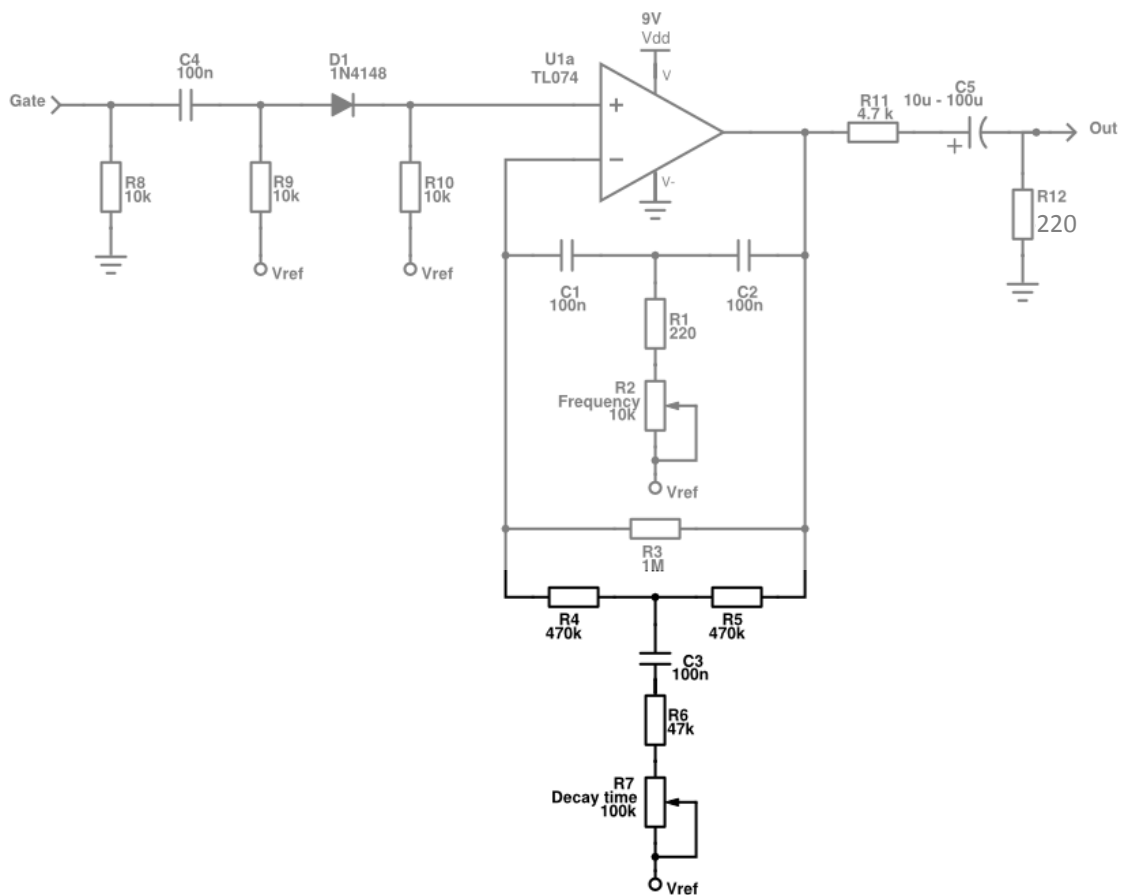
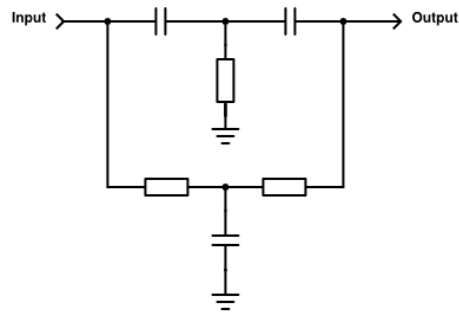
## A bit about how it works


---

At the heart of the circuit is this funny thing:



It's called a 'Twin-T' notch filter, because the drawing has kind of two 'T' shapes. It's not the easiest to analyze, but a rough idea of the function is this: low frequencies can pass through the lower part (through the resistors), and high frequencies can pass through the upper part (through the capacitors). Somewhere in between is a frequency that passes half through the lower, and half through the upper leg, but comes out with opposite phases. These cancel at the output, creating a notch.

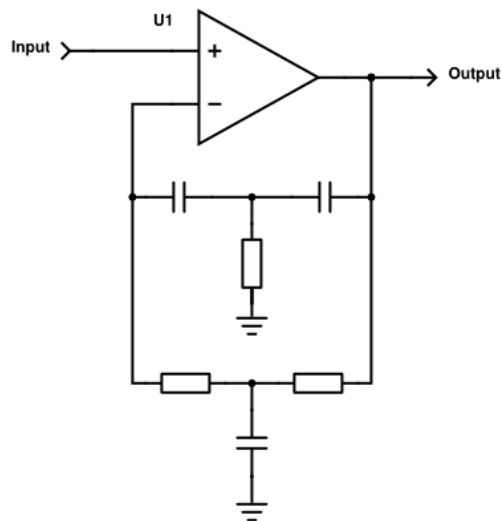Next comes a nice trick: put the filter in the feedback loop of an opamp. This basically 'inverts' the notch filter to a bandpass filter (the opamp will do whatever it can to make the + and - input equal. But at the notch frequency, it has to drive the filter very hard to get anything happening at the - input at all).



Like this it would oscillate at the output, because the notch filter is near perfect. In the main circuit, the 'decay time' resistor makes it less perfect on purpose, adjusting how 'resonant' the circuit is.

Finally, it is just a matter of 'kicking' the filter with a spike at the input, just like you would kick a real drum. It oscillates, but slowly decays back to zero.

## Connecting to other gear

So, you built the project, and the bass drum is working well enough that you want to use it with other gear. That's easy, but there are a few things to take care of.

### The trigger input


The trigger input is designed for 4.5V trigger signals, but any trigger input up to 30V can be used safely. The trigger can come for example from a drum computer or sequencer with 'gate' out, from an Arduino, or even a 'click track' from DAW software.

### The output

**Note:** *Be careful connecting self-built projects to inputs of other gear (sound cards, amplifiers, mixers...). It's possible to blow up the inputs!*

If built exactly as shown, the bass drum output gives a voltage swing of up about +/- 25 mV. That is a safe voltage for most equipment such as amplifier. Nevertheless, always turn the volume and input gain of your amp or mixer completely down before connecting, and then slowly turn it up while playing the drum until you hear something.

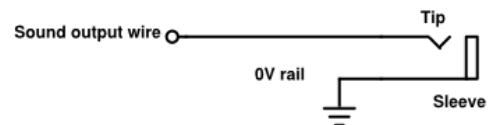If the output of the bass drum is too quiet, you can increase the value of R12 in steps until you are happy with the result. For most cases, 1k should be enough.




The picture on the right shows how to connect a 3.5mm or 6mm jack socket to the output. Always connect the signal (sound output wire) as well as the ground (0V rail)!
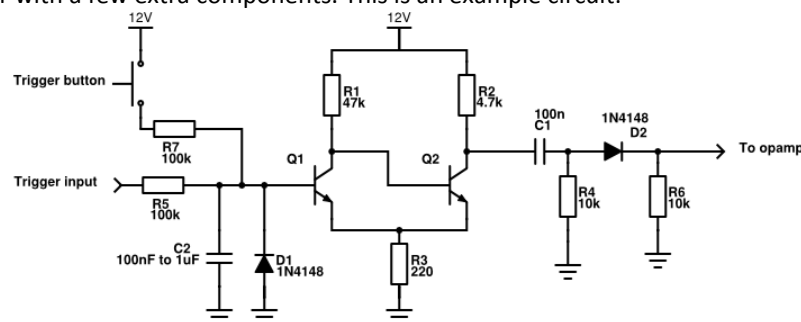
### Making a eurorack module

This goes beyond the scope of this workshop, but if you want to make this into a eurorack (or other) module, I would recommend a few changes:

- In eurorack you can power the opamp with +/- 12V, and you don't need Vref. Leave out the Vref circuit, and use ground everywhere instead of Vref. Also the ground points still go to ground.
- Modular synthesizers use larger signal voltages. You can use quite a large value for R12, such as 4.7k or 10k, if you want to connect the output to a modular synth.
- The trigger input is safe to use, but the output level depends on the trigger voltage. It is possible to make a cleaner trigger with a few extra components. This is an example circuit:



This replaces R8-R4, C4 and D1 in the main circuit. Transistors Q1 and Q2 can be 2N3904 or BC547.